

Chapter 14 Section 4

Define Electric Circuit:

What are the three parts of an electric circuit?

- 1.
- 2.
- 3.

Name three different types of loads.

- 1.
- 2.
- 3.

What is a switch used for in a circuit?

*The two types of circuits are **series and parallel** circuits.*

Define Series Circuit:

Illustrate a series circuit.

Give one use for a series circuit.

Define Parallel Circuit:

Illustrate a parallel circuit.

Give one use for a parallel circuit